

Analyze the circuit below and determine the following:

- a) What is the equivalent resistance of the entire circuit?
- b) What is the current being drawn from the battery?
- c) What is the power being dissipated in the 9 ohm resistor?

